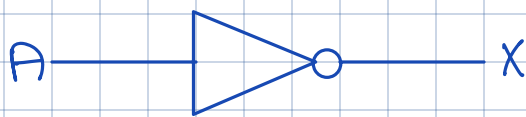



The inverter / NOT Gate:



$$\hookrightarrow X = \bar{A}$$


A	X = \bar{A}
0	1
1	0

↳ Example Waveform:

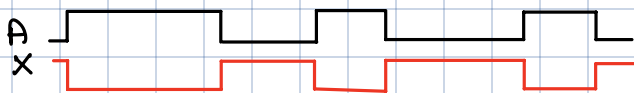

↳ A group of inverters can be used to form I's complement.

The AND Gate:

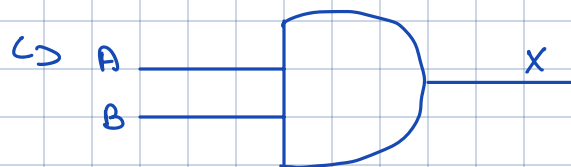


$$\hookrightarrow X = A \cdot B$$


A	B	X = A · B
0	0	0
0	1	0
1	0	0
1	1	1

↳ Used as a selective mask.

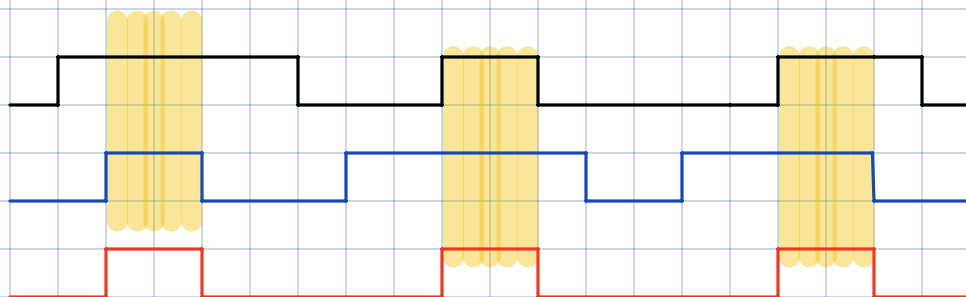↳ To select certain bits & discard other.




OR Gate:

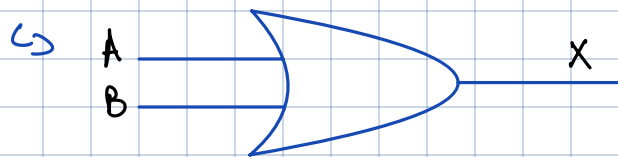


↪ $X = A + B$

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

↪ Used to set some bits to 1.

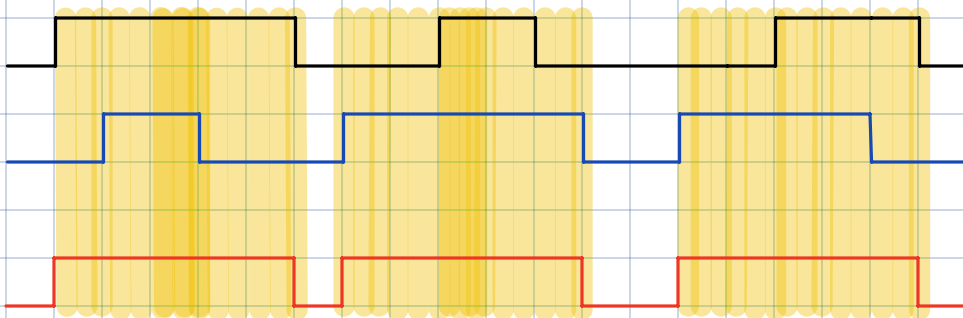


NAND Gate:

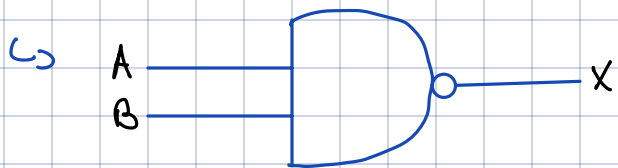


↪ $X = \overline{A \cdot B}$

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

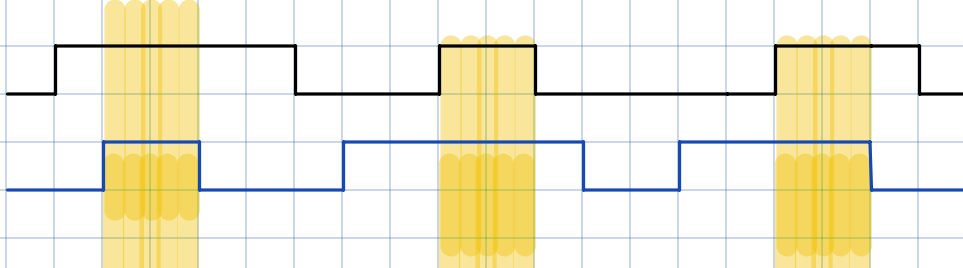


- ↳ It is an universal gate.
- ↳ All other Basic gates can be constructed from it.


1. NOT Gate:

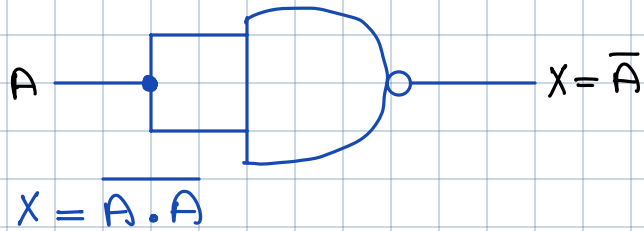


2. AND gate:

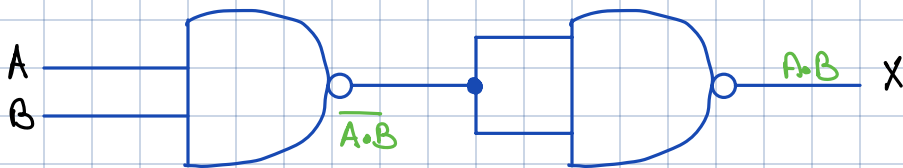

3. OR Gate:

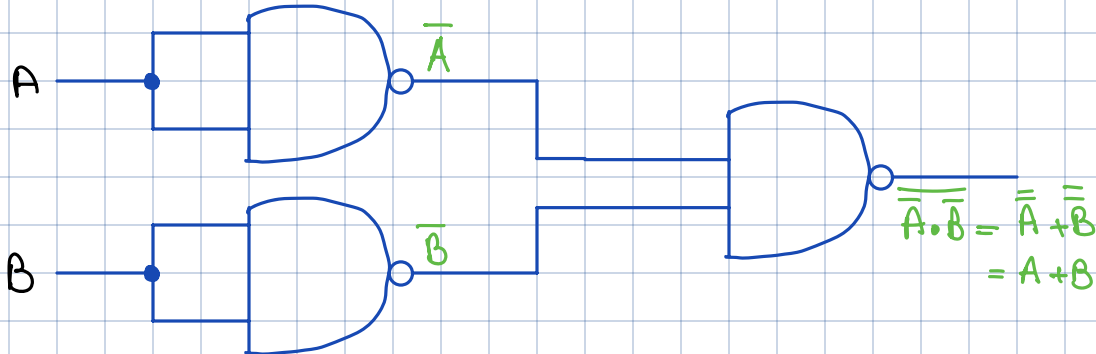


NOR Gate:

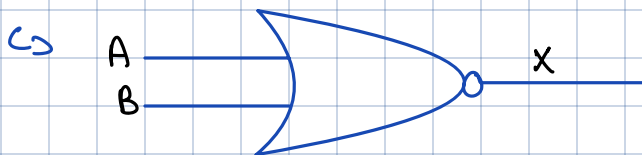


↳

A	B	$X = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

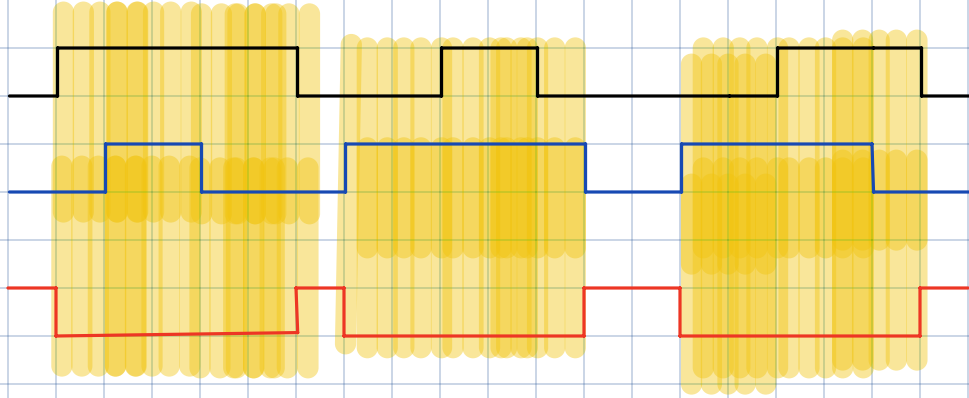

↳ Can be used to make the basic gates:

1. NOT gate:

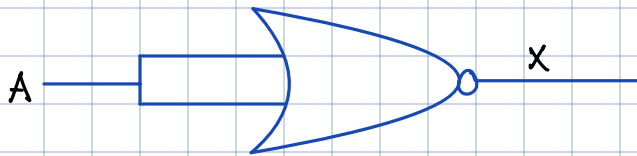

$$\hookrightarrow X = \overline{A+A}$$


2. OR gate:

$$A+B = \overline{\overline{A+B}}$$




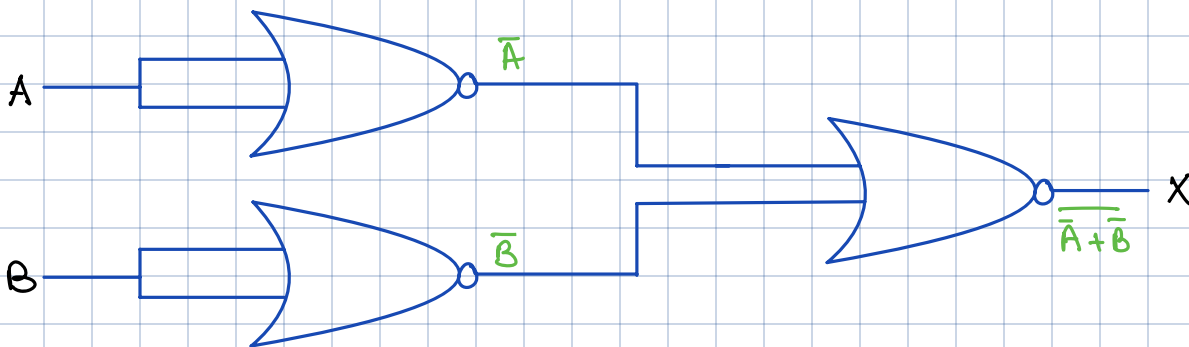3. AND gate:


$$\hookrightarrow A \cdot B = \overline{\overline{A+B}} = \overline{\overline{A} \cdot \overline{B}} = A \cdot B$$



XOR gate:

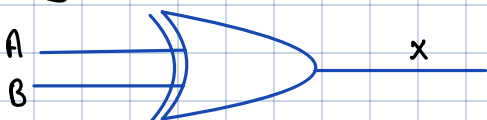



A	B	$X = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

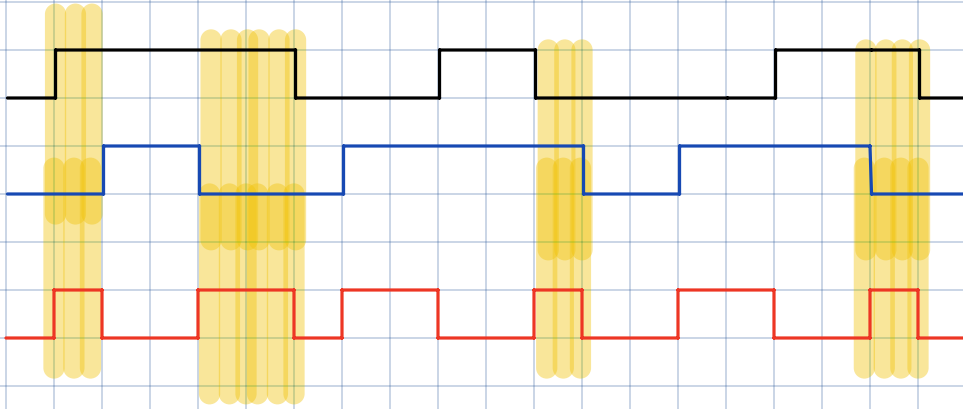

XNOR gate:

↪

A	B	$X = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

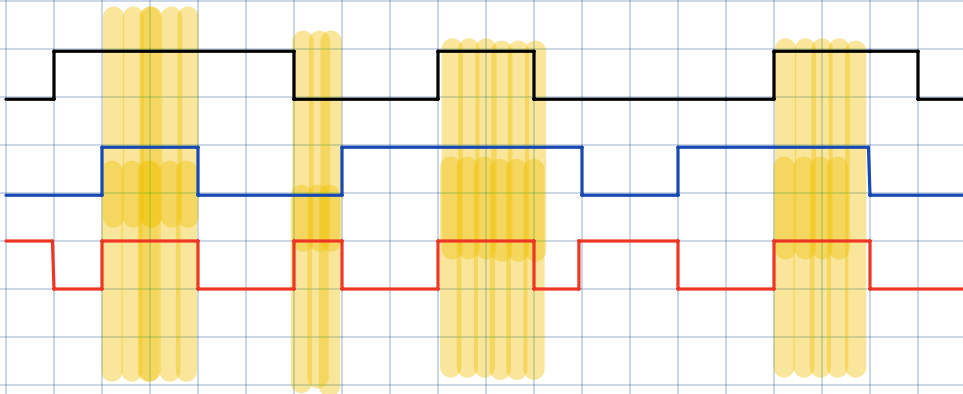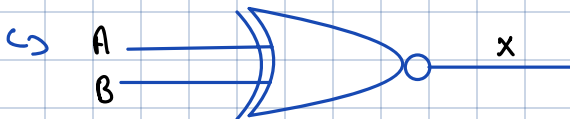

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	0	0	0	0
10	1	1	0	0

$$K1 = \bar{A}$$

$$K2 = \bar{B}\bar{C}$$

$$K = \bar{A} + \bar{B}\bar{C}$$

A	B	C	D	
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0